
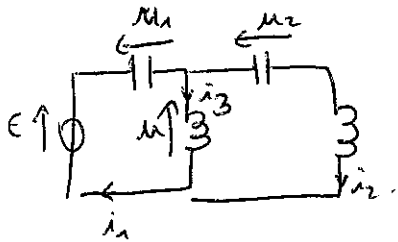


4)

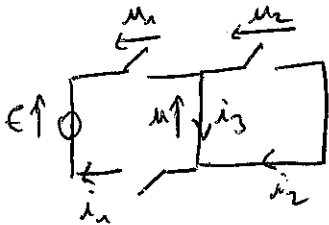

À  $t=0^-$ :



- \*  $u_1(0^-) = 0$  (fil)
  - \*  $i_1(0^-) = 0$  (int ouvert)
  - \*  $i_2(0^-) = 0$  (int ouvert)
- }  $\Rightarrow i_3(0^-) = 0$  (loi des nœuds)

- \*  $u_2(0^-) = 0$  (loi des mailles à droite).
- \*  $u_1(0^-) = 0$  (condensateur déchargé).

→ Continuités:


- Tension dans condensateur :  $u_1(0^+) = 0 / u_2(0^+) = 0$
- Intensité dans bobine :  $i_3(0^+) = 0 / \underline{i_2(0^+) = 0}$

À  $t=0^+$ :

\* Loi des nœuds :  $\underline{i_1(0^+) = 0}$


\* Loi des mailles :  $u(0^+) + u_1(0^+) = E \Rightarrow \underline{u(0^+) = E}$

$t \rightarrow +\infty$ :

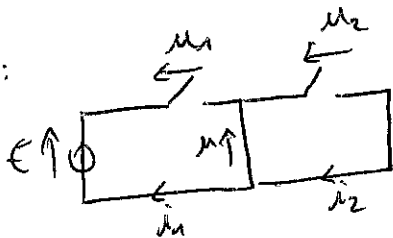


$\left\{ \begin{array}{l} i_1(\infty) = 0 \\ i_2(\infty) = 0 \\ u(\infty) = 0 \text{ (fil)} \end{array} \right\}$  int ouvert.

5)

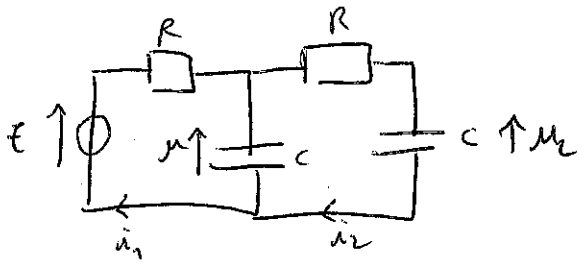

À  $t=0^-$ :

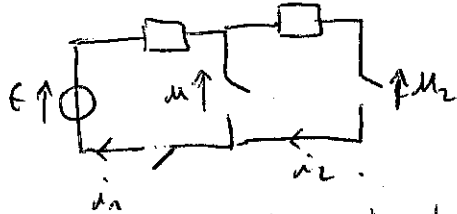


\*  $u_2(0^-) = 0$   
 \*  $u(0^-) = 0$  } déchargés d'après l'énoncé.

Par continuité de la tension aux bornes des C :

\*  $u_2(0^+) = 0$   
 \*  $u(0^+) = 0$

À  $t=0^+$ :

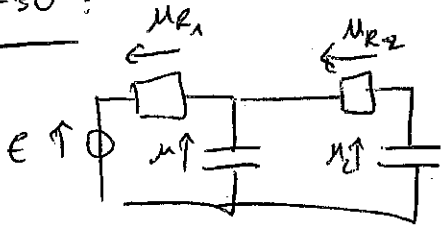


\* Loi des mailles (à droite) :

$\rightarrow u_{R_2}(0^+) = 0 \rightarrow$  Loi d'Ohm :  $i_2(0^+) = 0$

\* Loi des mailles (à gauche) :

$u_{R_1}(0^+) = E \Rightarrow$  Loi d'Ohm :  $i_1(0^+) = \frac{E}{R}$


$t \rightarrow \infty$  :

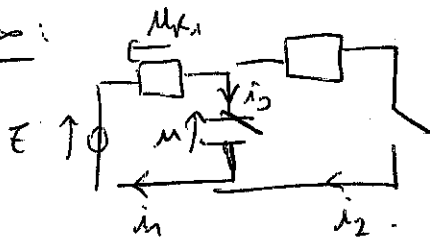


$i_2(\infty) = 0$   
 $i_3(\infty) = 0$  } loi des nœuds :  $i_1(\infty) = 0$

Ohm :  $u_{R_1}(\infty) = 0 \Rightarrow u(\infty) = E$  d'après la loi des mailles.

6)

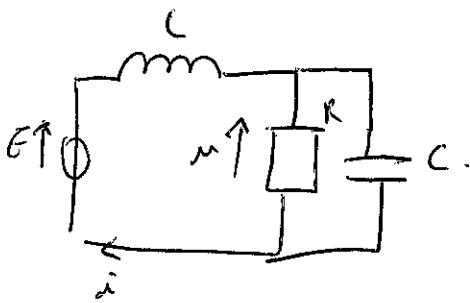

À  $t=0^-$ :

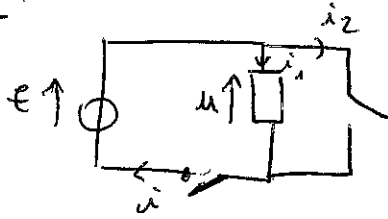


\*  $i(0) = 0$  (interrupteur ouvert)  
 \*  $i_2(0) = 0$  (idem)

Loi des noeuds:  $i_1(0^+) = 0$   
 ↓  
 Loi d'Ohm:  $u(0^+) = 0$

Continuités:



→ Tension dans C:  $u(0^+) = 0$   
 → Intensité dans L:  $i(0^+) = 0$

$t \rightarrow \infty$ :

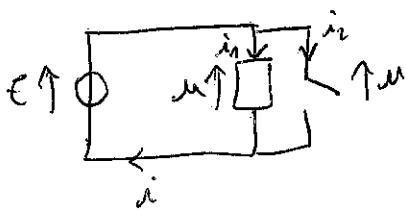

\* Boucles:  $u = E$   
 \*  $i_2(\infty) = 0$  (int ouvert)  $\Rightarrow i_1 = i_2$   
 \* Loi d'Ohm:  $i_1(\infty) = \frac{u(\infty)}{R} = \frac{E}{R} = i(\infty)$

7)

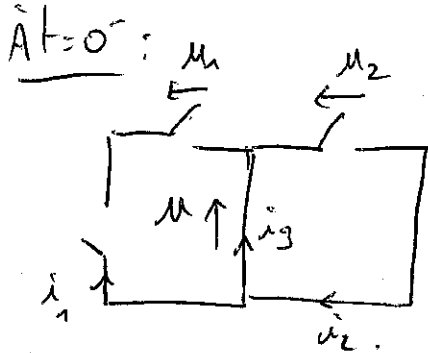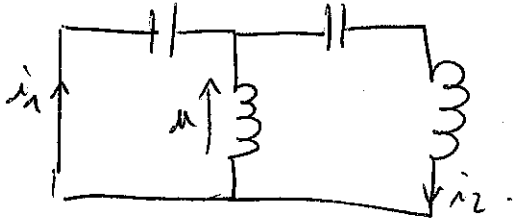

\*  $i_1(0^-) = 0$  (interrupteur ouvert) } loi des nœuds ;  $i_3(0^-) = 0$ .  
 \*  $i_2(0^-) = 0$

\*  $u_1(0^-) = E$  (énergie).


Continuités:

$-u_1(0^+) = E$

$-i_1(0^+) = 0$

$-i_3(0^+) = 0$


$\hat{A}t = 0^+ :$

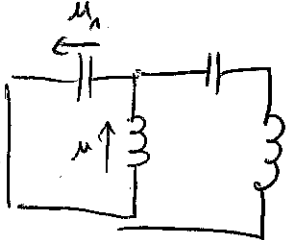

\* loi des nœuds:  $i_1(0^+) = 0$

\* boucle (gauche):  $u_1(0^+) - u_1(0^-) = E$


$t \rightarrow \infty :$

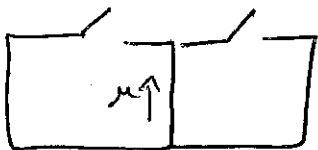


$u \rightarrow 0$  (fil)

$i_1 \rightarrow 0$  (int ouvert)

$i_2 \rightarrow 0$  (int ouvert)

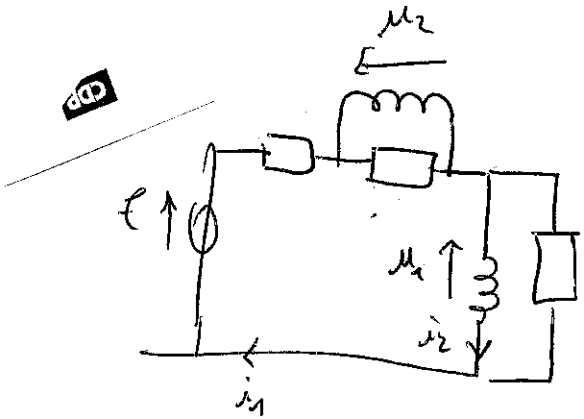

$t=0^-$ :

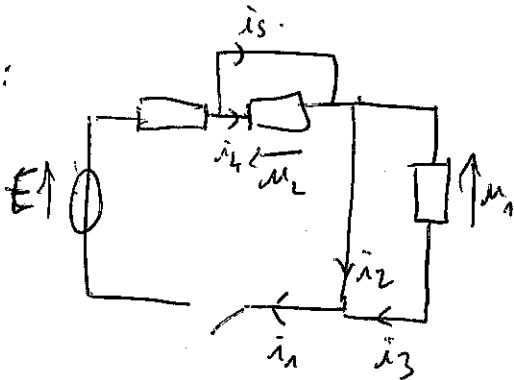


- \*  $\mu_1(0^-) = 0$  (fil)  $\Rightarrow$  Ohm:  $i_2(0^-) = 0$ .
- \*  $i_1(0^-) = 0$  (int ouvert)
- \* Nœuds:  $i_2(0^-) + i_3(0^-) = i_1(0^-)$   
 $\Rightarrow i_2(0^-) = 0$ .

- \*  $\mu_2(0^-) = 0$  (fil)  $\rightarrow$  Ohm:  $i_4(0^-) = 0$
- \* Nœuds:  $i_5(0^-) = 0$

Continuités:

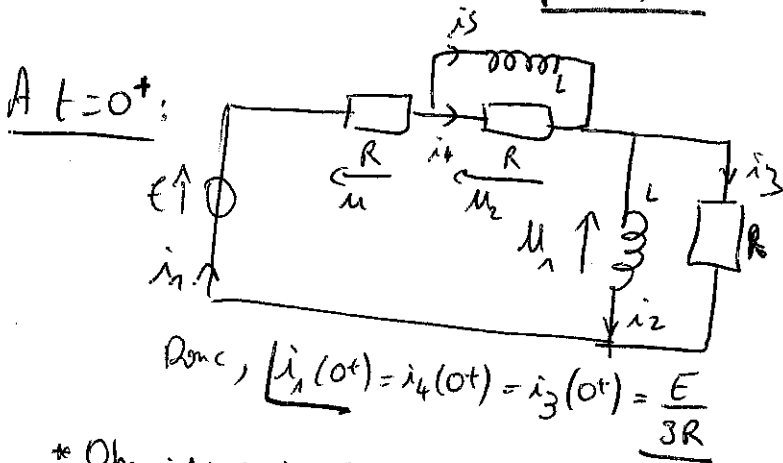$\rightarrow$  Bobine intensités:  $\begin{cases} \dot{i}_5(0^+) = 0 \\ \dot{i}_2(0^+) = 0 \end{cases}$




- \* Nœuds:  $i_1(0^+) = i_4(0^+) = i_3(0^+)$
- \* Mailles:  $\mu_1(0^+) + \mu_2(0^+) + u(0^+) = E$
- \* Ohm:  $R i_3(0^+) + R i_4(0^+) + R i_1(0^+) = E$

Donc,  $i_1(0^+) = i_4(0^+) = i_3(0^+) = \frac{E}{3R}$

- \* Ohm:  $\mu_1(0^+) = R i_3(0^+) = \frac{E}{3}$
- $\mu_2(0^+) = R i_4(0^+) = \frac{E}{3}$

$t \rightarrow \infty$ :

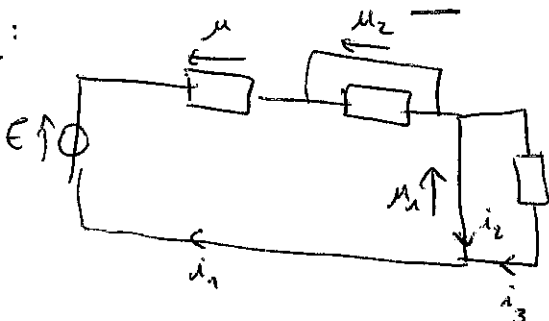

$t \rightarrow \infty$   
 $\mu_1 \rightarrow 0$   
 $\mu_2 \rightarrow 0$  (fils)

- \* Mailles:  $\mu = E \Rightarrow$  Ohm:  $i_1 \rightarrow \frac{E}{R}$
- \* Ohm:  $i_3 \rightarrow 0 \Rightarrow$  Nœuds:  $i_2 \rightarrow i_1 \rightarrow \frac{E}{R}$